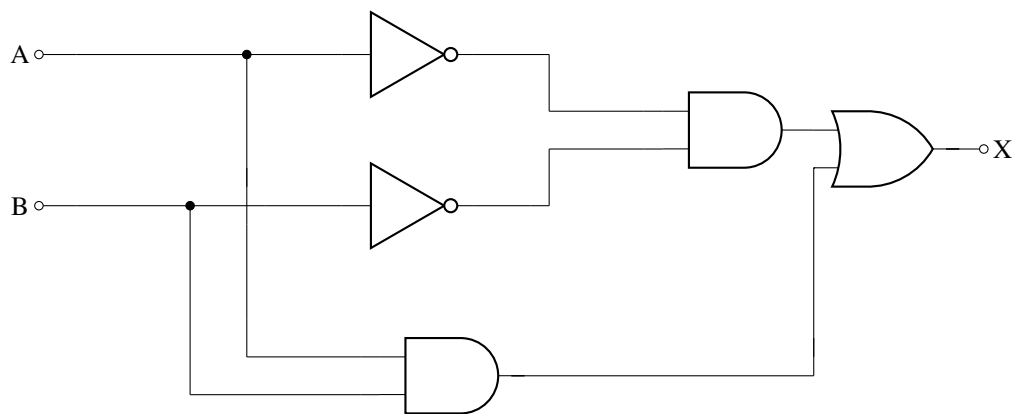


## Gate IN2017, 20

Pandrangi Aditya Sriram

FWC22249

1.  $A$  and  $B$  are logical inputs and  $X$  is the logical output shown in the figure. The output  $X$  is related to  $A$  and  $B$  by (GATE IN 2017)



- A.  $X = \bar{A}B + \bar{B}A$
- B.  $X = AB + \bar{B}A$
- C.  $X = AB + (\bar{B})(\bar{A})$
- D.  $X = (\bar{A})(\bar{B}) + \bar{B}A$